

NEELU SARASWAT IBHATLA (SRNS2)

1. (i) A logic variable can take one of 2 values:


- true/1/high

- false/0/low


(ii) A logic gate takes one or more inputs and performs a logic function on them, returning an output.

✓ (iii) A logic function takes one or more boolean inputs and returns a boolean output.


2. NOT

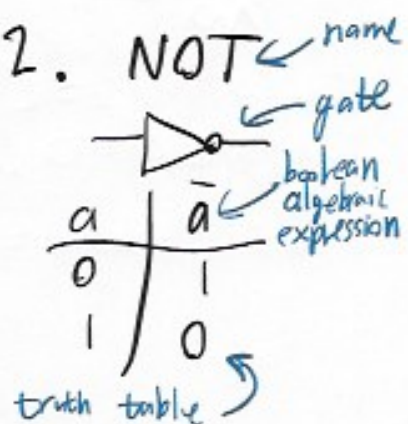

OR

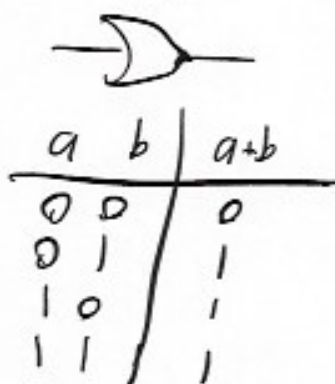


AND

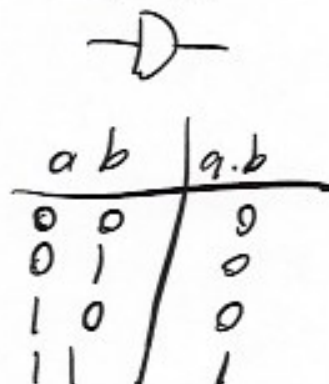


4 more:

NOR

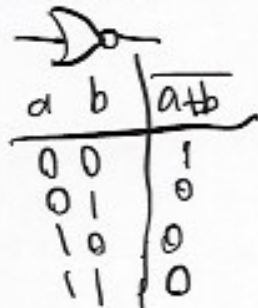


NAND

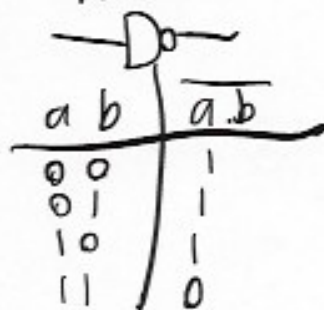

XOR




XNOR

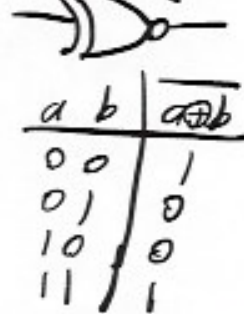

3. A logic function with more than 3 logic gates does more than 3 simple operations.

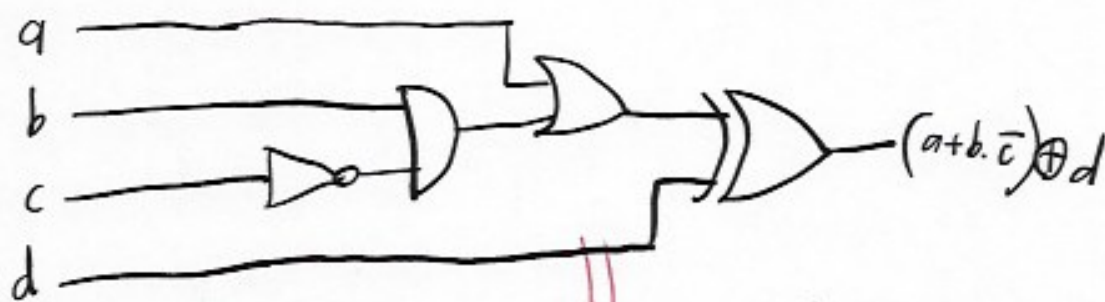Example: $(a + b \cdot \bar{c}) \oplus d$



a	b	c	d	$(a + b \cdot \bar{c}) \oplus d$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Check again

$$\begin{aligned}
 & (a + b \cdot \bar{c}) \oplus d \\
 &= (a \oplus d) + (b \cdot \bar{c} \oplus d) \\
 & \text{NO} \\
 & a=0, b=1, c=1 \\
 & (0 + 1) \oplus 1 = 0 \\
 & (0 \oplus 1) + (1 \oplus 0) = 1
 \end{aligned}$$

4. 1. a

a	b	\bar{a}	$\overline{a \cdot b}$	\bar{b}	$\overline{a \cdot \bar{b}}$	$x[(\overline{a \cdot b}) \cdot (\overline{a \cdot \bar{b}})]$
0	0	1	1	1	1	0
0	1	1	0	0	1	1
1	0	0	1	1	0	1
1	1	0	1	0	1	0

②

a	b	\bar{a}	$\overline{a+b}$	\bar{b}	$\overline{a+\bar{b}}$	$x[(\overline{a+b}) + (\overline{a+\bar{b}})]$
0	0	1	0	1	0	1
0	1	1	0	0	1	0
1	0	0	1	1	0	0
1	1	0	0	0	0	1

2. (a) $LHS = a \cdot b \cdot c + a \cdot b \cdot \bar{c} = (a \cdot b) \cdot (c + \bar{c}) = (a \cdot b) \cdot 1 = a \cdot b = RHS \checkmark$

(b) $LHS = a \cdot (\bar{a} + b) = a \cdot \bar{a} + a \cdot b = 0 + a \cdot b = a \cdot b = RHS \checkmark$

(c) $LHS = a \cdot b + \bar{a} \cdot c = (a \cdot b \cdot c + a \cdot b \cdot \bar{c} + \bar{a} \cdot b \cdot c + \bar{a} \cdot \bar{b} \cdot c) + a \cdot b \cdot c + \bar{a} \cdot b \cdot c$
 $= a \cdot b \cdot (c + \bar{c}) + \bar{a} \cdot c \cdot (b + \bar{b}) + b \cdot c \cdot (a + \bar{a})$
 $= (a \cdot b + \bar{a} \cdot c + b \cdot c) + a \cdot \bar{a}$
 $= a \cdot (\bar{a} + b) + c \cdot (\bar{a} + b)$
 $= (a + c) \cdot (\bar{a} + b) = RHS \checkmark$

$$\begin{aligned}
 \textcircled{d} \quad LHS &= (a+c) \cdot (a+d) \cdot (b+c) \cdot (b+d) \\
 &= ((a+c) \cdot (a+d)) \cdot ((b+c) \cdot (b+d)) \\
 &= (a \cdot a + a \cdot c + a \cdot d + c \cdot d) \cdot (b \cdot b + b \cdot c + b \cdot d + c \cdot d) \\
 &= (a + a \cdot c + a \cdot d + c \cdot d) \cdot (b + b \cdot c + b \cdot d + c \cdot d) \\
 &= (a + c \cdot d)(b + c \cdot d) \\
 &= a \cdot b + a \cdot c \cdot d + b \cdot c \cdot d + c \cdot d \\
 &= a \cdot b + c \cdot d = RHS \quad \checkmark
 \end{aligned}$$



$$\begin{aligned}
 3. \quad Z &= \overline{(\bar{a} + a \cdot b \cdot c)} + b \quad \xrightarrow{\text{(De Morgan)}} (\bar{a} + a \cdot b \cdot c) \cdot \bar{b} = \bar{a} \bar{b} + a b \bar{b} c = \\
 &= \bar{a} \cdot \overline{(a \cdot b \cdot c)} + b \\
 &= a \cdot (\bar{a} + \bar{b} + \bar{c}) + b \\
 &= a \cdot \bar{a} + a \cdot \bar{b} + a \cdot \bar{c} + b \\
 &= a \cdot \bar{b} + a \cdot \bar{c} + b \\
 &= a \cdot \bar{b} \cdot c + a \cdot \bar{b} \cdot \bar{c} + a \cdot b \cdot \bar{c} + \cancel{a \cdot \bar{b} \cdot \bar{c}} + a \cdot b \cdot c + \cancel{a \cdot \bar{b} \cdot c} + \cancel{a \cdot b \cdot \bar{c}} + \cancel{a \cdot b \cdot c} \\
 &= a \cdot \bar{b} \cdot c + a \cdot \bar{b} \cdot \bar{c} + a \cdot b \cdot \bar{c} + a \cdot b \cdot c + \bar{a} \cdot b \cdot c \\
 &= a \cdot \bar{b} \cdot (c + \bar{c}) + a \cdot b \cdot (c + \bar{c}) + \bar{a} \cdot b \cdot c \\
 &= a \cdot \bar{b} + a \cdot b + \bar{a} \cdot b \cdot c \\
 &= \underline{\underline{a + \bar{a} \cdot b \cdot c}}
 \end{aligned}$$




4. ab

	cd	00	01	11	10
00		0	0	0	0
01		0	0	1	0
11		0	1	1	1
10		0	0	1	0

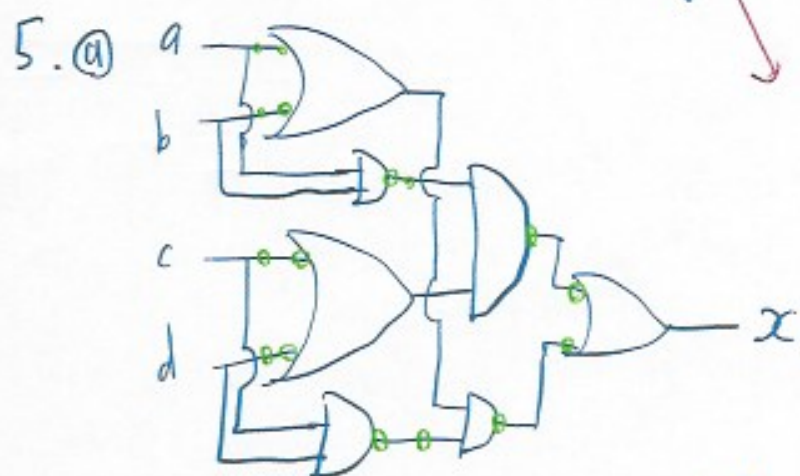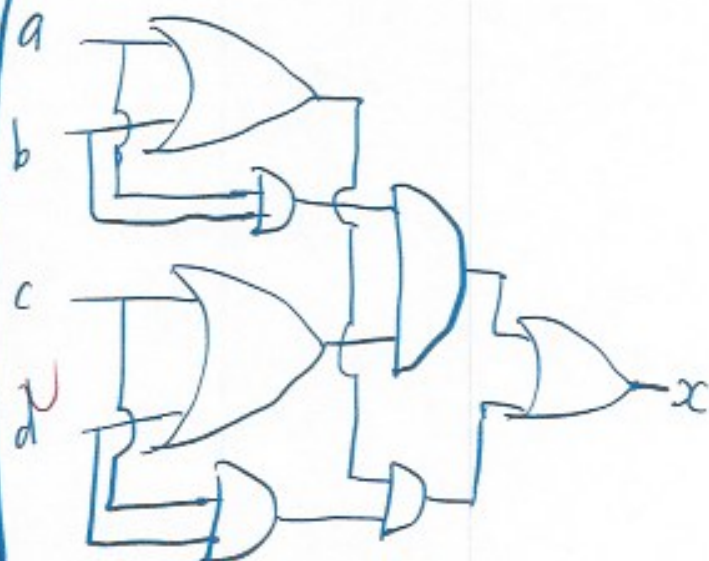
$$\begin{aligned}
 x &= a \cdot b \cdot d + a \cdot b \cdot c \\
 &\quad + b \cdot c \cdot d + a \cdot c \cdot d \\
 &= a \cdot b (c + d) + c \cdot d (a + b)
 \end{aligned}$$


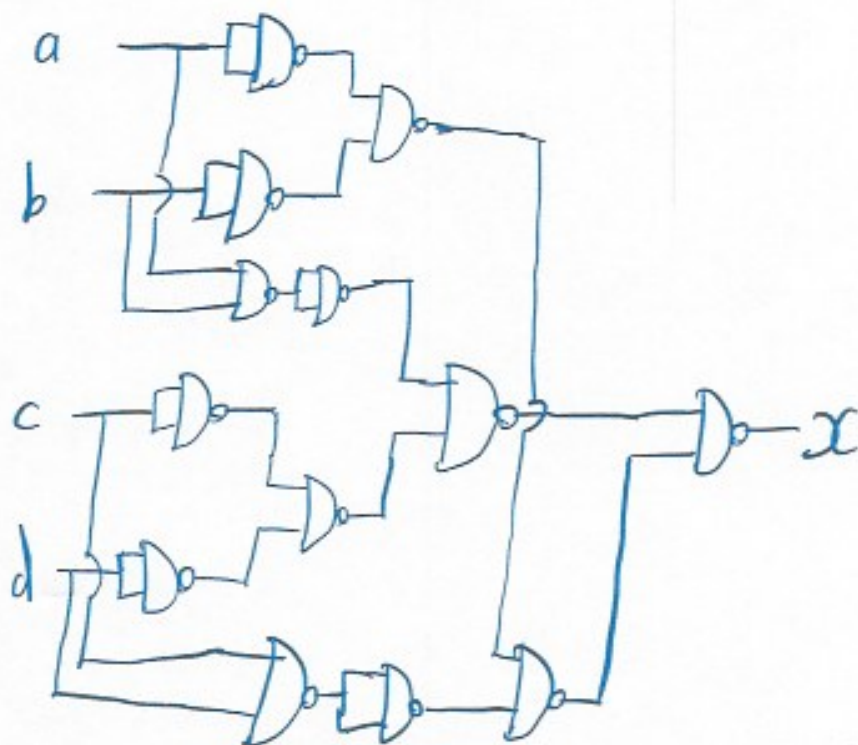
$$\overline{a}b\overline{c}d + \overline{a}b\overline{c}d + \overline{b}c\overline{a}d + \overline{a}c\overline{b}d$$



(b)

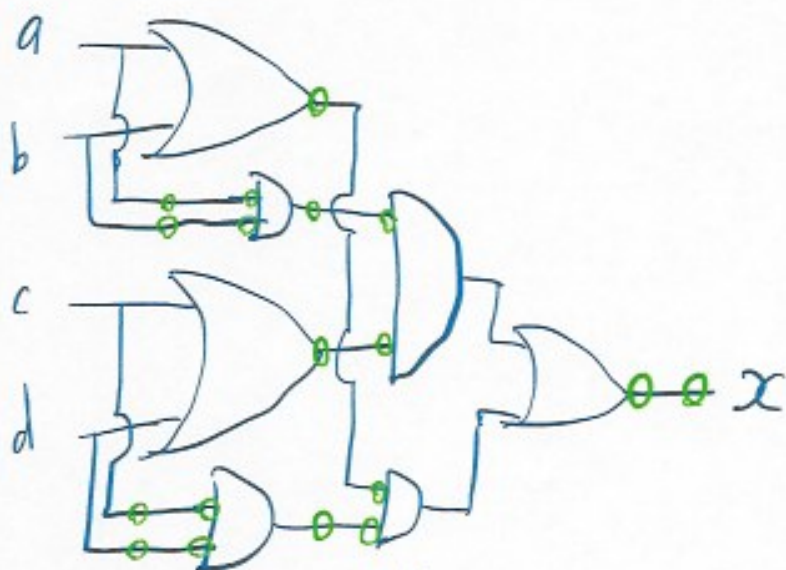


$$V = (a+b)(a+c)(a+d)(b+c) \\ (b+d)(c+d)$$


//

$$V = \frac{\overline{a+b} + \overline{a+c} + \overline{a+d} + \overline{b+c} \\ + \overline{b+d} + \overline{c+d}}{}$$

? //

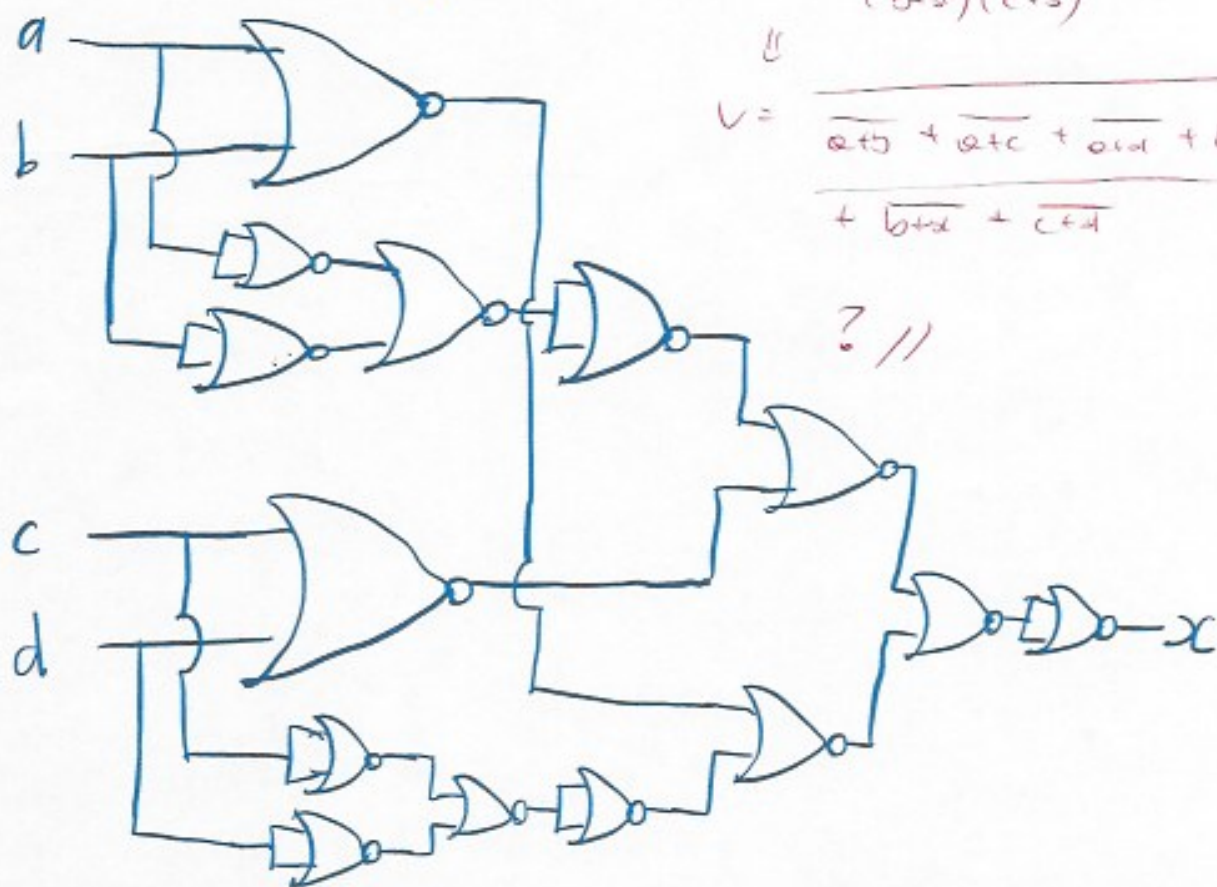

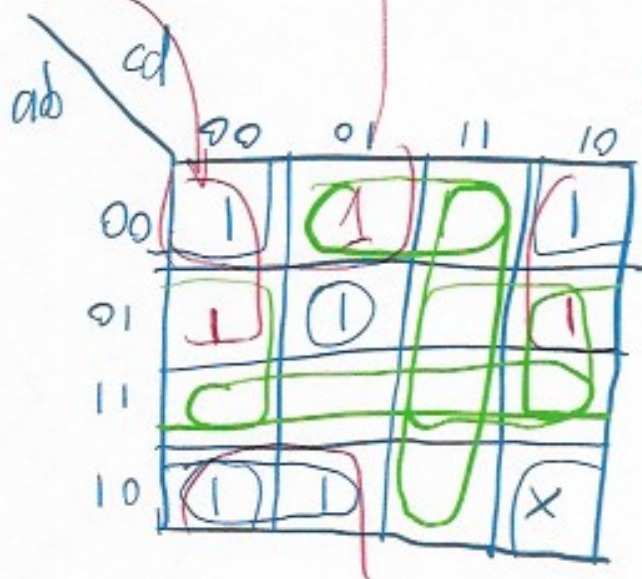b. $f = \bar{a} \cdot \bar{d} + \bar{b} \cdot \bar{c} + \bar{a} \cdot b \cdot \bar{c} \cdot d$
 don't care: $a \cdot \bar{b} \cdot c \cdot \bar{d}$




$\bar{a} \cdot \bar{c} + \bar{b} \cdot \bar{c} + \bar{a} \cdot \bar{d}$
 $f = \bar{a} \cdot \bar{c} + \bar{b} \cdot \bar{c} + \bar{a} \cdot \bar{d}$




$f = \bar{b} \cdot d + \bar{a} \cdot \bar{b} \cdot \bar{c} + \bar{a} \cdot b \cdot \bar{c} \cdot d$

$\bar{f} = a \cdot b + b \cdot c + c \cdot d + b \cdot d + \bar{a} \cdot \bar{b} \cdot d$


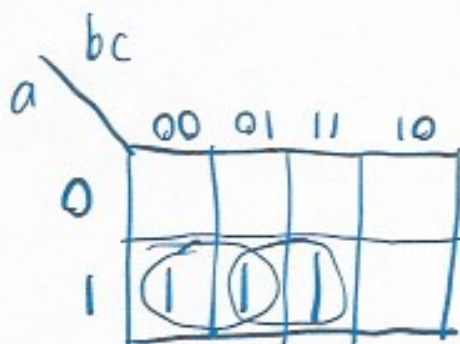
7. $f = a \cdot \bar{b} \cdot \bar{c} + a \cdot \bar{b} \cdot c + a \cdot b \cdot c$



$f = a \cdot \bar{b} + a \cdot c$ ✓

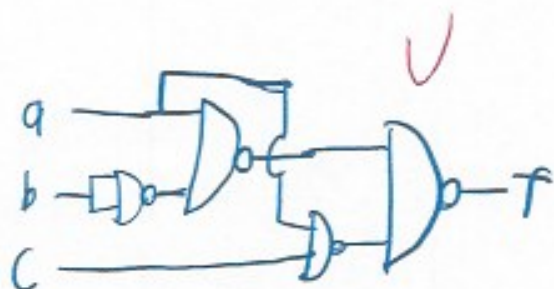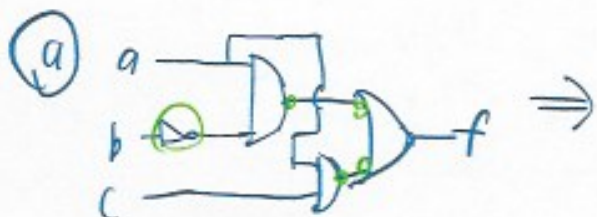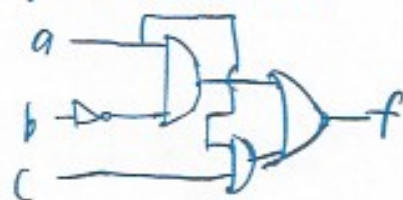

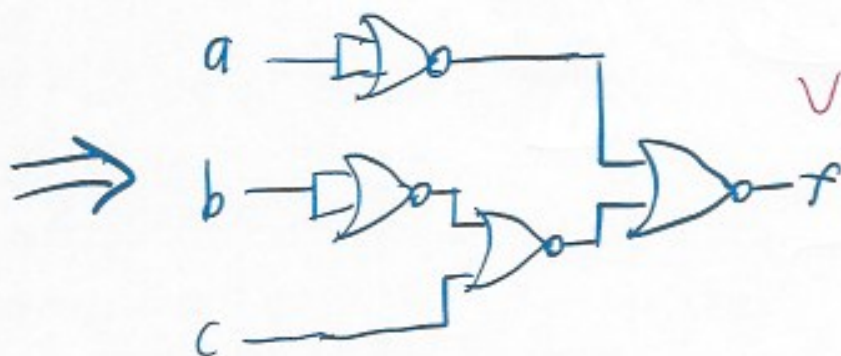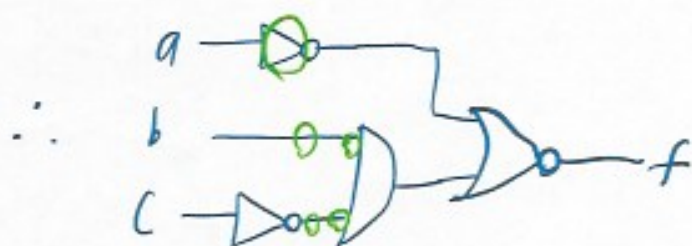⑥ $\bar{f} = \bar{a} + b \cdot \bar{c}$ $f = \bar{\bar{f}}$



5.

AB		CD			
		00	01	11	10
CD	00			1	
	01	1	1	1	
	11	1	1	1	1
	10			1	1

(i) $f = A \cdot B \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot D + A \cdot B \cdot \bar{C} \cdot D + \bar{A} \cdot B \cdot C \cdot D + A \cdot B \cdot C \cdot D + A \cdot \bar{B} \cdot C \cdot D + A \cdot B \cdot C \cdot \bar{D} + A \cdot \bar{B} \cdot C \cdot \bar{D}$

(ii) $f = A \cdot B + B \cdot D + A \cdot C$ ✓

AB		CD			
		00	01	11	10
CD	00			1	1
	01		1	1	
	11	1	1	1	
	10			1	

(i) $f = A \cdot B \cdot \bar{C} \cdot \bar{D} + A \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot D + A \cdot B \cdot \bar{C} \cdot D + \bar{A} \cdot B \cdot C \cdot D + A \cdot B \cdot C \cdot D + A \cdot B \cdot C \cdot \bar{D}$

(ii) $f = A \cdot B + B \cdot D + A \cdot \bar{C} \cdot \bar{D}$ ✓

AB \ CD	00	01	11	10
00			1	1
01	1	1		1
11	1			1
10	1			

$$(i) f = A \cdot B \cdot \bar{C} \cdot \bar{D} + A \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot D + \bar{A} \cdot B \cdot \bar{C} \cdot D + A \cdot \bar{B} \cdot \bar{C} \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot D + A \cdot \bar{B} \cdot C \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot \bar{D}$$

$$(ii) f = A \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot \bar{C} \cdot D + \bar{B} \cdot D + \bar{A} \cdot \bar{B} \cdot C \\ = \bar{C} (A \cdot \bar{D} + \bar{A} \cdot D) + \bar{B} (D + \bar{A} \cdot C) \\ = (A \oplus D) \cdot \bar{C} + \bar{B} (D + \bar{A} \cdot C) \quad \checkmark$$

AB \ CD	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1			1

$$(i) f = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} + A \cdot \bar{B} \cdot \bar{C} \cdot \bar{D} + \bar{A} \cdot B \cdot \bar{C} \cdot D + A \cdot B \cdot \bar{C} \cdot D + \bar{A} \cdot \bar{B} \cdot C \cdot D + \bar{A} \cdot B \cdot C \cdot D + A \cdot \bar{B} \cdot C \cdot D + A \cdot B \cdot C \cdot D$$

$$(ii) f = B \cdot D + \bar{B} \cdot \bar{D} \quad \checkmark$$

(iii)

AB \ CD	00	01	11	10
00			0	
01	0		0	0
11	0	0	0	0
10			0	

$$\bar{f} = A \cdot B + C \cdot D + \bar{B} \cdot D + \bar{A} \cdot \bar{D}$$

$$\bar{f} = (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) \cdot (B + \bar{D}) \cdot (\bar{A} + \bar{D})$$

$$f = (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) \cdot (B + \bar{D}) \cdot (\bar{A} + \bar{D})$$

already covered

$$6. F(A, B, C, D) = \sum m(0, 2, 5, 6, 7, 8, 10, 12, 13, 14, 15)$$

Implication Table

0000	0111	1101
0010	1000	1110
0101	1010	1111
0110	1100	

	Column 1	Column 2	Column 3
0	0000 ✓	00-0 *	-11- * ok
2	0010 ✓	-000 *	11-- * ok
5	0101 *	011- ✓	-1-1
8	1000 ✓	1-10 *	1--0
5	0110 ✓	110- ✓	--10
10	1010 ✓	111- ✓	-0-0
12	1100 ✓		
7	0111 ✓		
13	1101 ✓		
14	1110 ✓		
15	1111 ✓		

$$\text{Ans: } \bar{B}\bar{D} + BD + C\bar{D} + A\bar{D}$$

Prime Implicant Chart

	0	2	5	6	7	8	10	12	13	14	15
8,10 $\boxed{0, 2 (00-0)}$	*	*									
2,6,10,14 $\boxed{0, 8 (-000)}$	*					*					
7,13,15 $\boxed{5 (0101)}$			*								
8,12 $\boxed{10, 14 (1-10)}$						*				*	
✓ $\boxed{6, 7, 14, 15 (-11-)}$			*	*						*	*
✓ $\boxed{12, 13, 14, 15 (11--)}$							*	*	*	*	*

$$\begin{aligned} \therefore F(A, B, C, D) &= \bar{A} \cdot \bar{B} \cdot \bar{D} + \bar{B} \cdot \bar{C} \cdot \bar{D} \\ &+ \bar{A} \cdot B \cdot \bar{C} \cdot D \\ &+ A \cdot C \cdot \bar{D} + B \cdot C \\ &+ A \cdot B \end{aligned}$$

7. A half adder takes 2 input bits (a and b), and outputs a sum bit and a carry out bit. A full adder takes a carry in bit in addition to a and b, and outputs a sum bit and a carry out bit.


Half adder




$$C_{out} = a \cdot b$$

$$Sum = a \oplus b$$

a	b	sum	C _{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

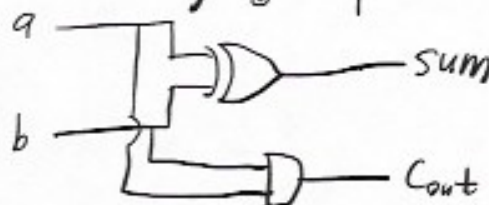


Full adder

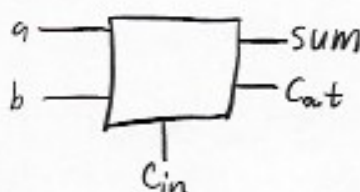

a	b	C _{in}	sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\begin{aligned}
 Sum &= \bar{C}_{in} (a \oplus b) + C_{in} (\bar{a} \cdot \bar{b} + a \cdot b) \\
 &= \bar{C}_{in} (a \oplus b) + C_{in} ((a+b) \cdot (\bar{a} + \bar{b})) \\
 &= \bar{C}_{in} (a \oplus b) + C_{in} (a \cdot \bar{a} + a \cdot \bar{b} + \bar{a} \cdot b + \bar{b} \cdot \bar{b}) \\
 &= \bar{C}_{in} (a \oplus b) + C_{in} (\bar{a} \cdot b + a \cdot \bar{b}) \\
 &= C_{in} (\bar{a} \oplus \bar{b}) + \bar{C}_{in} (a \oplus b) \\
 &= a \oplus b \oplus C_{in}
 \end{aligned}$$

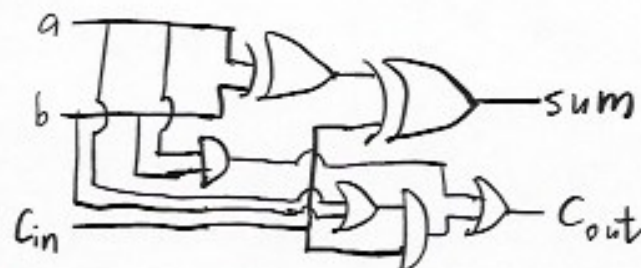

ab	00	01	11	10
C _{out}	0	0	1	0
C _{in}	0	1	1	0

$$\begin{aligned}
 C_{out} &= a \cdot b + b \cdot C_{in} + a \cdot C_{in} \\
 &= a \cdot b + C_{in} (a + b)
 \end{aligned}$$