

## NEELU SARASWATI BHATLA (SRNS2)

1. A synchronous FSM has states, and its current state determines its next state. The two types are:

- Mealy machine - Inputs and outputs appear on transitions
- Moore machine - Only inputs appear on transitions

## 2. SR-FF

SR-Latch diagram




Truth table

S	R	Q'	Q
0	0	Q	Q
0	1	0	1
1	0	1	0
1	1	0	0

Excitation Table

Q	Q'	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

State Diagram

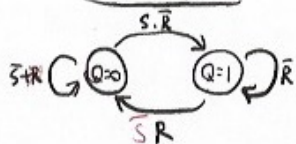


## JK-FF

Truth Table

J	K	Q'	Q
0	0	Q	Q
0	1	0	1
1	0	1	0
1	1	Q'	Q

State Diagram

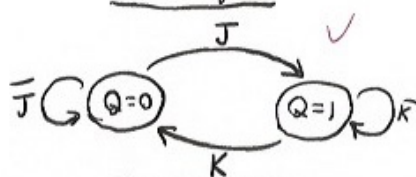

Excitation Table

Q	Q'	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

## D-FF


Truth Table

D	Q'	Q
0	0	1
1	1	0

Excitation Table

Q	Q'	D
0	0	0
0	1	1
1	0	0
1	1	1

State Diagram

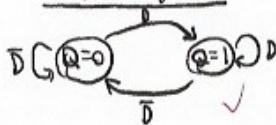

# T-FF



## Truth Table

T	Q'	Q'
0	Q	Q
1	Q	Q

## Excitation Table

Q	Q'	T
0	0	1
0	1	0
1	0	0
1	1	1

## State Diagram

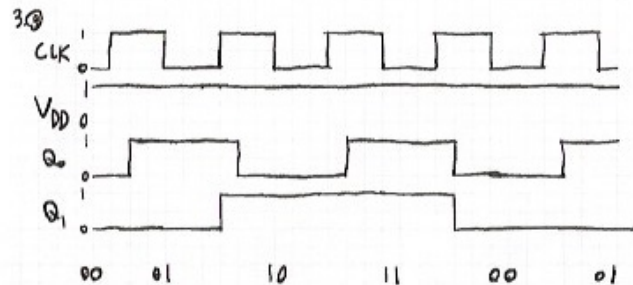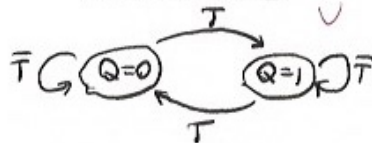



Q <sub>0</sub> Q <sub>1</sub> Q <sub>2</sub>	Q <sub>0</sub> ' Q <sub>1</sub> ' Q <sub>2</sub> '	T <sub>0</sub> T <sub>1</sub> T <sub>2</sub>
0 0 0	1 1 1	1 1 1
0 0 1	1 1 0	1 1 0
0 1 0	1 0 1	1 0 1
0 1 1	1 0 0	1 0 0
1 0 0	0 1 1	0 1 1
1 0 1	0 1 0	0 1 0
1 1 0	0 0 1	0 0 1
1 1 1	0 0 0	0 0 0

$$T_0 = 1$$


$$T_1 = Q_0$$

$$T_2 = Q_0 \cdot Q_1$$

(Continued on next page)

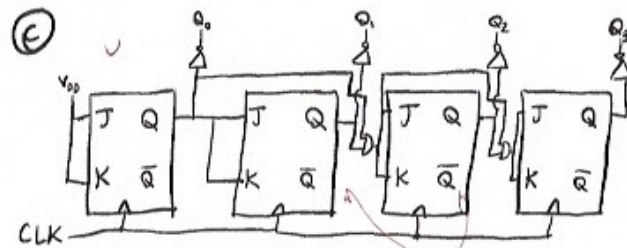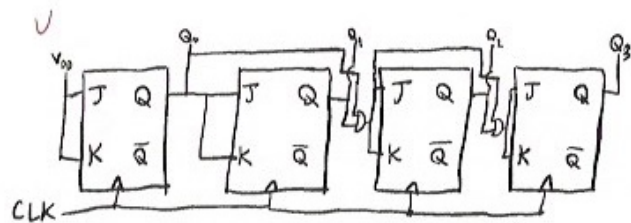

or you could use  $\bar{Q}$  outs

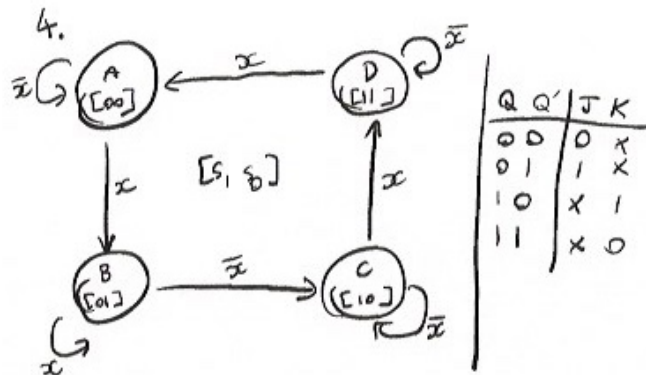

✓

$S_1$	$S_0$	$x$	$S_1'$	$S_0'$	$J_1$	$K_1$	$J_0$	$K_0$
0	0	0	0	0	0	x	0	x
0	0	1	0	1	0	x	1	x
0	1	0	1	0	1	x	x	1
0	1	1	0	1	0	x	x	0
1	0	0	1	0	x	0	0	x
1	0	1	1	1	x	0	1	x
1	1	0	1	1	x	0	x	0
1	1	1	0	0	x	1	x	1

$$J_1$$

	$s_0$	00	01	11	10
$x$		0	0	1	1
0		0	0	1	1
1		0	0	1	1

$$J_1 = s_0 \cdot \bar{x} \checkmark$$

$$K_1$$

	$s_0$	00	01	11	10
$x$		0	1	1	0
0		1	1	0	0
1		1	1	0	0

$$K_1 = s_0 \cdot x \checkmark$$

$$J_0$$


	$s_0$	00	01	11	10
$x$		0	1	1	0
0		0	1	1	0
1		0	1	1	0

$$J_0 = x \checkmark$$

$$K_0$$

	$s_0$	00	01	11	10
$x$		0	1	1	0
0		1	1	0	0
1		1	1	0	0
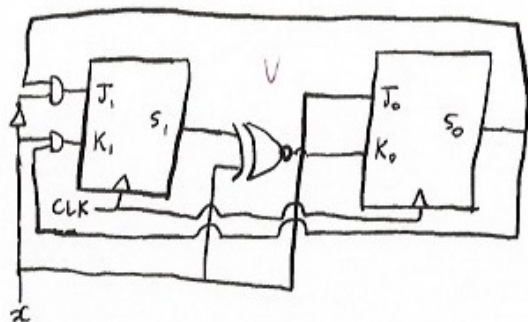
$$K_0 = \bar{s}_1 \cdot \bar{x} + s_1 \cdot x \\ = s_1 \oplus x \checkmark$$



$$5. J_0 = \bar{Q}_1 \quad J_1 = Q_0 \\ K_0 = 1 \quad K_1 = 1$$

Q	Q'	J	K
0	0	0	1
0	1	1	1
1	0	1	0
1	1	0	0

$$K=1 \Rightarrow$$

Q	Q'	J
0	0	0
0	1	1
1	0	0
1	1	1

$\Rightarrow$  When  $J=0, Q'=0$   
When  $J=1, Q'=\bar{Q}$

If  $Q_0=Q_1=0$  at the start

CLOCK CYCLE	$Q_1$	$Q_0$	$J_1$	$J_0$
0	0	0	0	1
1	0	1	1	1
2	1	0	0	0
3	0	0	0	1
4	0	1	1	1
5	1	0	0	0

cfv mod 3


This goes through  $(Q_1, Q_0) = (0,0), (0,1)$  and  $(1,0) \checkmark$   
repeats.  $Q_1$  and  $Q_0$  are each on for one clock cycle (out of phase with each other) and out for two. Now  $(Q_1, Q_0) = (1,1)$  be investigated.

If  $Q_1 = Q_0 = 1$ ,

CLOCK CYCLE	$Q_1$	$Q_0$	$J_1$	$J_0$
0	1	1	1	0
1	0	0	1	1

... and this then goes into the cycle from before.

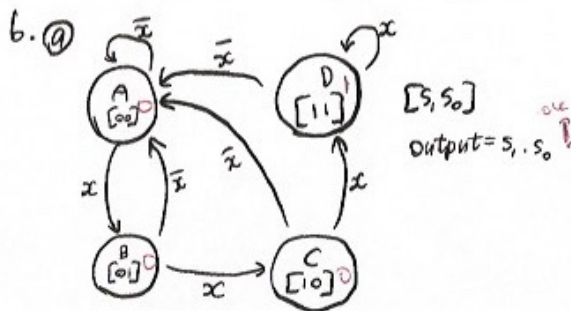$\therefore Q_0$  is on for one clock cycle and off for two, and so is  $Q_1$ , but is one cycle after  $Q_0$ .



b) Moore machine

①

$s_1$	$s_0$	$x$	$s_1'$	$s_0'$	$J_1$	$K_1$	$J_0$	$K_0$	$D_1$	$D_0$
0	0	0	0	0	0	x	0	x	0	0
0	0	1	0	1	0	x	1	x	0	1
0	1	0	0	0	0	x	x	1	0	0
0	1	1	1	0	1	x	x	1	1	0
1	0	0	0	0	x	1	0	x	0	0
1	0	1	1	1	x	0	1	x	1	1
1	1	0	0	0	x	1	x	1	0	0
1	1	1	1	1	x	0	x	0	1	1

② JK-FFs

$J_1$  ok

$s_1 s_0$	00	01	11	10
0	0	x	x	x
1	x	x	x	x

$K_1$  ok

$s_1 s_0$	00	01	11	10
0	x	x	1	0
1	x	x	x	x

$J_1 = s_0 \cdot x$  ✓  
 $K_1 = \bar{x}$  ✓


$J_0$  ok

$s_1 s_0$	00	01	11	10
0	x	x	x	x
1	x	x	x	x

$K_0$  ok


$s_1 s_0$	00	01	11	10
0	x	1	1	0
1	x	x	x	x

$J_0 = x$  ✓  
 $K_0 = \bar{x} + s_1$  ✓

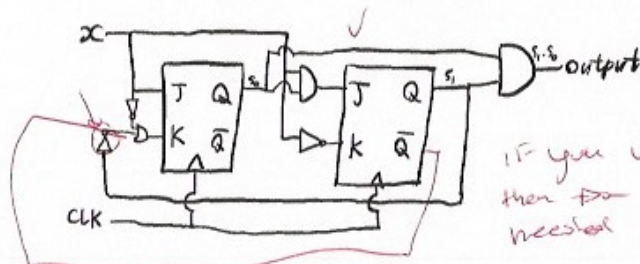






# D-FFs

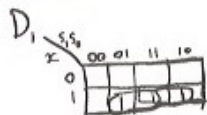
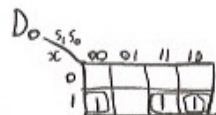
$$D_1 = s_0 \cdot x + s_1 \cdot x \\ = (s_0 + s_1) \cdot x$$


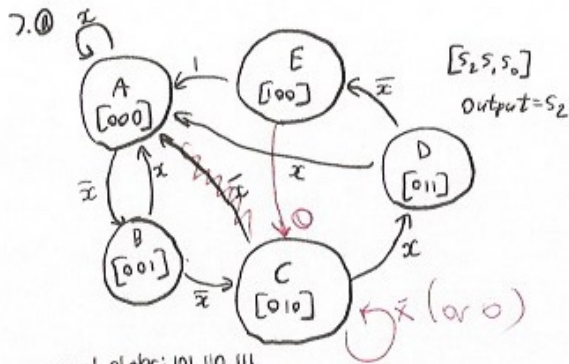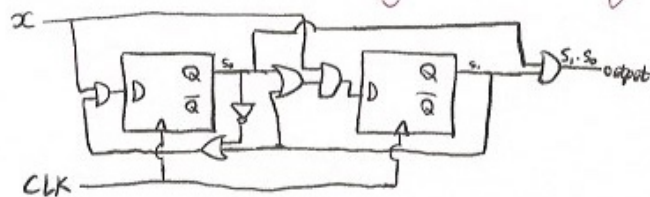
$$D_0 = s_1 \cdot x + \bar{s}_0 \cdot x \\ = (s_1 + \bar{s}_0) \cdot x$$



unused states: 101, 110, 111

(b)

Current State	Next State	
	x=0	x=1
A	B	A
B	C	A
C	<del>A</del>	D
D	E	A
E	<del>A</del>	A


There aren't any redundant states here...

8. @


$Q_2$	$Q_1$	A	$Q_1'$	$Q_1'$	$D_2$	$D_1$
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	1	1	0	1	0
1	0	0	0	1	0	1
1	0	1	1	1	1	1
1	1	0	0	1	0	1
1	1	1	1	1	1	1

$$D_2 = A \\ D_1 = Q_2$$



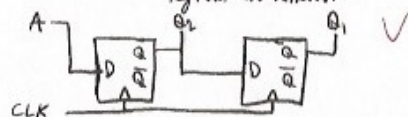
∴ This can be implemented by connecting the D flip-flops in the form of a shift register as follows:



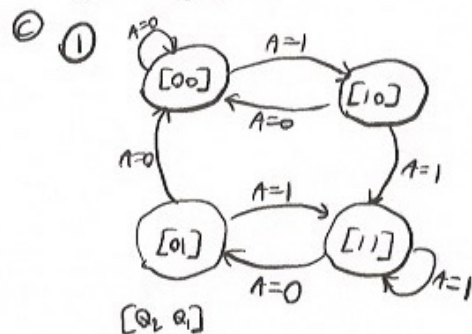⑥ As the clock rate increases, the D-flip flops have less time to both switch as that is a propagation delay in a shift register, so output errors are more likely, and the dotted line transitions are less likely to happen.




$Q_2$	$Q_1$	$A$	$Q_2'$	$Q_1'$	$D_2$	$D_1$
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	1	1	1	1	1
1	0	0	0	0	0	0
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1

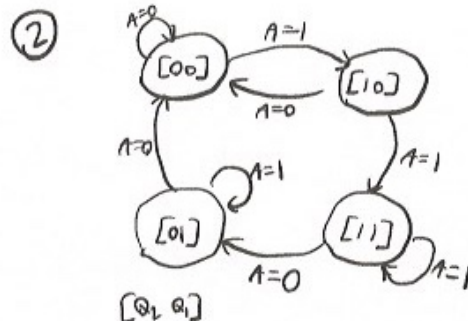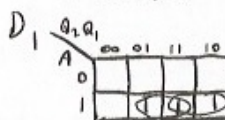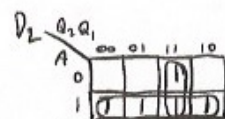


$Q_2$	$Q_1$	$A$	$Q_2'$	$Q_1'$	$D_2$	$D_1$
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	1	0	1	0	1
1	0	0	0	0	0	0
1	0	1	1	1	1	1
1	1	0	1	1	1	1
1	1	1	1	1	1	1



③

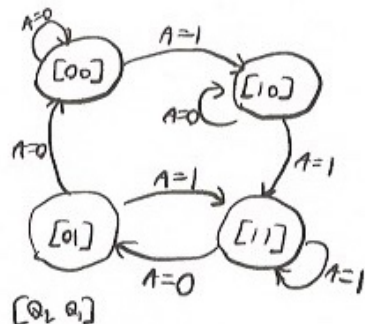

$Q_2$	$Q_1$	$A$	$Q_2'$	$Q_1'$	$D_2$	$D_1$
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	0	1	0	1
1	1	1	1	1	1	1

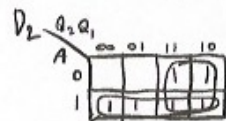


$$D_2 = A + Q_2$$

$$D_1 = A \cdot Q_2 + A \cdot Q_1$$

$$= A \cdot (Q_2 + Q_1)$$

④

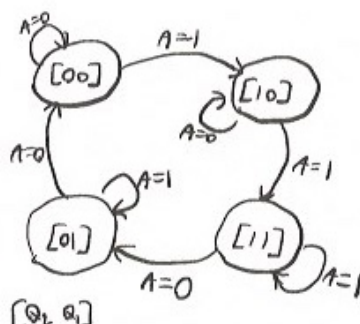

$Q_2$	$Q_1$	$A$	$Q_2'$	$Q_1'$	$D_2$	$D_1$
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	1	0	1	0	1
1	0	0	1	0	1	0
1	0	1	1	1	1	1
1	1	0	0	1	0	1
1	1	1	1	1	1	1



$$D_2 = Q_2 + A \cdot \bar{Q}_1$$

$$D_1 = A \cdot Q_2 + A \cdot Q_1$$

$$= A \cdot (Q_2 + Q_1)$$